

18CS 33

ANALOG AND DIGITAL ELECTRONICS

MODULE 4

VHDL, LATCHES AND FLIP-FLOPS

Mahesh Prasanna K.
Dept. of CSE, VCET.

INTRODUCTION TO VHDL

- * **VHDL** stands for **VHSIC-HDL** (*Very High Speed Integrated Circuit-Hardware Description Language*).
- * **VHDL** is a hardware description language that is used to describe the behavior and structure of digital systems.
- * **VHDL** is a general-purpose hardware description language which can be used to describe and simulate the operation of a wide variety of digital systems, ranging in complexity from a few gates to an interconnection of many complex integrated circuits.
- * **VHDL** was originally developed to allow a uniform method for specifying digital systems. The VHDL language became an IEEE standard in 1987, and it is widely used in industry. IEEE published a revised VHDL standard in 1993.

-
- * **VHDL** can describe a digital system at several different levels—*behavioral*, *data flow*, and *structural*. For example,
 - * A binary adder could be described at the *behavioral level* in terms of its function of adding two binary numbers, without giving any implementation details.
 - * The same adder could be described at the *data flow level* by giving the logic equations for the adder.
 - * Finally, the adder could be described at the *structural level* by specifying the interconnections of the gates which make up the adder.


VHDL DESCRIPTION OF COMBINATIONAL CIRCUITS

- * In VHDL, a signal assignment statement has the form:

* $C \leq A \text{ and } B \text{ after } 5 \text{ ns};$ `signal_name <= expression [after delay];`

- * A VHDL signal (are *concurrent*) is used to describe a signal in a physical system .
- * Square brackets indicate that after delay is *optional*.
- * If after delay is omitted, then the signal is scheduled to be updated after a *delta delay*, Δ (*infinitesimal delay*).
- * VHDL is *not case sensitive*.
- * VHDL *identifiers* may contain *letters, numbers, and the underscore character* .
- * An *identifier must start with a letter*, and it cannot end with an underscore.
- * VHDL statement can be continued over several lines.
- * anything following a *double dash* (--) is treated as a *comment*.
- * Words such as *and*, *or*, and *after* are reserved words (or *keywords*).

 - * The gate circuit of the following Figure has five signals: *A*, *B*, *C*, *D*, and *E*. The symbol “*<=*” is the *signal assignment operator* which indicates that the value computed on the right-hand side is assigned to the signal on the left side.



* Dataflow Description

C <= *A and B after 5 ns*;

E <= *C or D after 5 ns*;

* Behavioral Description


E <= *D or (A and B)*;

* Structural Description

Gate1: AND2 port map (A, B, D);


Gate2: OR2 port map (C, D, E);

 Inverter with output
connected back
to the input



CLK <= not CLK after 10 ns;

* Bit & Vector

 


-- when A changes, these concurrent
-- statements all execute at the same time

`D <= A and B after 2 ns;`

`E <= not A after 1 ns;`

`F <= A or C after 3 ns;`

 

-- the hard way

`C(3) <= A(3) and B(3);`

`C(2) <= A(2) and B(2);`

`C(1) <= A(1) and B(1);`

`C(0) <= A(0) and B(0);`

-- the easy way

`C <= A and B;`

* Inertial Delay Model

A device with an inertial delay of D time units filters out output changes that would occur in less than or equal to D time units.

* Signal assignment statements containing “*after delay*” create what is called an *inertial delay model*.

* Consider a device with an inertial delay of D time units.

* If an input change to the device will cause its output to change, then the output changes D time units later.

* But, if the device receives two input changes within a period of D time units; the device output does not change in response to either input change.

* *Example:* Consider the signal assignment $C \leq A \text{ and } B \text{ after } 10 \text{ ns};$

Assume A and B are initially 1, and A changes to 0 at 15 ns, to 1 at 30 ns, and to 0 at 35 ns. Then C changes to 1 at 10 ns and to 0 at 25 ns, but C does not change in response to the A changes at 30 ns and 35 ns.

* Ideal (Transport) Delay Model


- * Output changes caused by input changes to a device exhibiting an ideal (transport) delay of D time units are delayed by D time units, and the output changes occur even if they occur within D time units.

- * The VHDL signal assignment statement that models ideal (transport) delay is
`signal_name <= transport expression after delay`

- * *Example:* consider the signal assignment $C \leq \text{transport } A \text{ and } B \text{ after } 10 \text{ ns};$

Assume A and B are initially 1 and A changes to 0 at 15 ns, to 1 at 30 ns, and to 0 at 35 ns. Then C changes to 1 at 10 ns, to 0 at 25 ns, to 1 at 40 ns, and to 0 at 45 ns. Note that the last two changes are separated by just 5 ns.

VHDL MODELS FOR MULTIPLEXERS

 

$$F = A'I_0 + AI_1$$

The corresponding VHDL statement is

```
F <= (not A and I0) or (A and I1);
```


MUX by a conditional signal assignment statement,

```
F <= I0 when A = '0' else I1;
```

The general form of a conditional signal assignment statement is

```
signal_name <= expression1 when condition1  
                else expression2 when condition2  
                [else expressionN];
```

Two Cascaded MUXes

 


```
F <= A when E = '1'  
      else B when D = '1'  
      else C;
```

* 4-to-1 MUX

$$F = A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3.$$
 
$$F \leq (\text{not } A \text{ and not } B \text{ and } I_0) \text{ or } (\text{not } A \text{ and } B \text{ and } I_1) \text{ or} \\ (A \text{ and not } B \text{ and } I_2) \text{ or } (A \text{ and } B \text{ and } I_3);$$




```
sel <= A&B;
-- selected signal assignment statement
with sel select
  F <= I0 when "00",
      I1 when "01",
      I2 when "10",
      I3 when "11";
```

```
F <= I0 when A = '0' and B = '0'
     I1 when A = '0' and B = '1'
     I2 when A = '1' and B = '0'
     I3;
```

The general form of a selected signal assignment statement is

```
with expression_s select
  signal_s <= expression1 [after delay-time] when choice1,
              expression2 [after delay-time] when choice2,
              ...
              [expression_n [after delay-time] when others];
```

VHDL MODULES

 


```
entity two_gates is
    port (A,B,D: In bit; E: out bit);
end two_gates;
architecture gates of two_gates is
    signal C: bit;
begin
    C <= A and B; -- concurrent
    E <= C or D; -- statements
end gates;
```

- When we describe a system in VHDL, we must specify an *entity* and *architecture* at the top level.
- The *entity* declaration gives the name “*two_gates*” to the module.
- The *port* declaration specifies the inputs and outputs to the module. *A*, *B*, and *D* are input signals of type bit, and *E* is an output signal of type bit.
- The *architecture* is named “*gates*”.
- The signal *C* is declared within the architecture because it is an internal signal. The two concurrent statements that describe the gates are placed between the keywords *begin* and *end*.

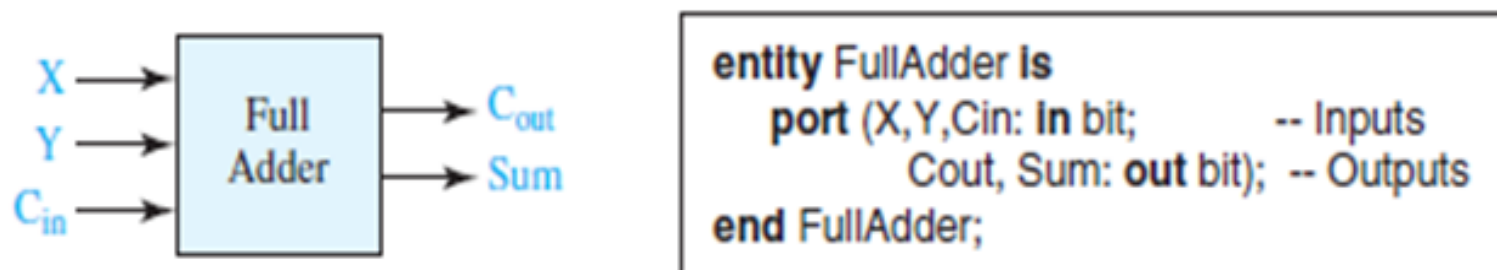Example: To write the entity and architecture for a full adder module.

The entity specifies the inputs and outputs of the adder module, as shown in the following Figure. The port declaration specifies that *X*, *Y* and *C_{in}* are input signals of type bit, and that *C_{out}* and *Sum* are output signals of type bit.



The operation of the full adder is specified by an architecture declaration:


```
architecture Equations of FullAdder is
begin
  -- concurrent assignment statements
  Sum <= X xor Y xor Cin after 10 ns;
  Cout <= (X and Y) or (X and Cin) or (Y and Cin) after 10 ns;
end Equations;
```

In this example, the architecture name (*Equations*) is arbitrary, but the entity name (*FullAdder*) must match the name used in the associated entity declaration.

The VHDL assignment statements for *Sum* and *C_{out}* represent the logic equations for the full adder.

Several other architectural descriptions such as a truth table or an interconnection of gates could have been used instead. In the *C_{out}* equation, parentheses are required around (*X and Y*) because VHDL does not specify an order of precedence for the logic operators.

* Four-Bit Full Adder

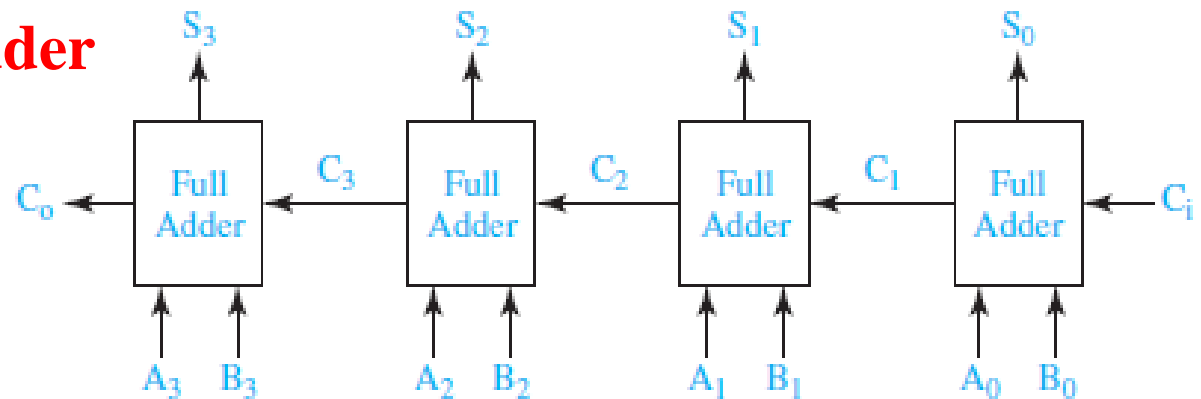

entity Adder4 is

```
    port (A, B: in bit_vector(3 downto 0); Ci: in bit;    -- Inputs  
          S: out bit_vector(3 downto 0); Co: out bit);    -- Outputs
```

end Adder4;

architecture Structure of Adder4 is

component FullAdder

```
    port (X, Y, Cin: in bit;    -- Inputs  
          Cout, Sum: out bit);  -- Outputs
```

end component;

signal C: bit_vector(3 downto 1);

begin -- instantiate four copies of the FullAdder

```
    FA0: FullAdder port map (A(0), B(0), Ci, C(1), S(0));
```

```
    FA1: FullAdder port map (A(1), B(1), C(1), C(2), S(1));
```

```
    FA2: FullAdder port map (A(2), B(2), C(2), C(3), S(2));
```


```
    FA3: FullAdder port map (A(3), B(3), C(3), Co, S(3));
```

end Structure;

Homework:

1] Write VHDL statements that represent the following circuit:

 - Write a statement for each gate.
- Write one statement for the whole circuit.



2] Draw the circuit represented by the following VHDL statements:

$F \leq E \text{ and } I;$


$I \leq G \text{ or } H;$

$G \leq A \text{ and } B;$

$H \leq \text{not } C \text{ and } D;$

3] Write

 - a complete VHDL module for a two-input NAND gate with 4-ns delay.
- Write a complete VHDL module for the following circuit that uses the NAND gate module of Part (a) as a component.







LATCHES & FLIP-FLOPS


- * Sequential switching circuits have the property that the *output depends not only on the present input but also on the past sequence of inputs.*
- * In effect, these circuits must be able to “*remember*” something about the past history of the inputs in order to produce the present output.
- * Latches and flip-flops are commonly used *memory devices* in sequential circuits.
- * Basically, latches and flip-flops are memory devices which
 - * *can assume one of two stable output states and*
 - * *have one or more inputs that can cause the output state to change.*

SET RESET LATCH

    
- * A simple latch can be constructed by introducing feedback into a NOR-gate circuit, as given in the following Figure (a).
- * As indicated, if the inputs are $S = R = 0$, the circuit can assume a stable state with $Q = 0$ and $P = 1$.



 
* The circuit is often drawn in cross-coupled form, as shown in Figure (a).



(a)

 

(b)

 


(c)

$$Q(t + \epsilon) = R(t)'[S(t) + Q(t)] = R(t)'S(t) + R(t)'Q(t)$$

$$\text{or } Q^+ = R'S + R'Q$$

$$P(t) = S(t)'Q(t) \text{ or}$$

$$P = S'Q'$$

 


(a) Q^+ map

S	R	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

(b) Truth table


$$Q^+ = S + R'Q$$

Inputs not allowed

 


Present State Q	Next State Q^+				Present Output P			
	SR 00	SR 01	SR 11	SR 10	SR 00	SR 01	SR 11	SR 10
0	0	0	0	1	1	1	0	0
1	1	0	0	1	0	0	0	0

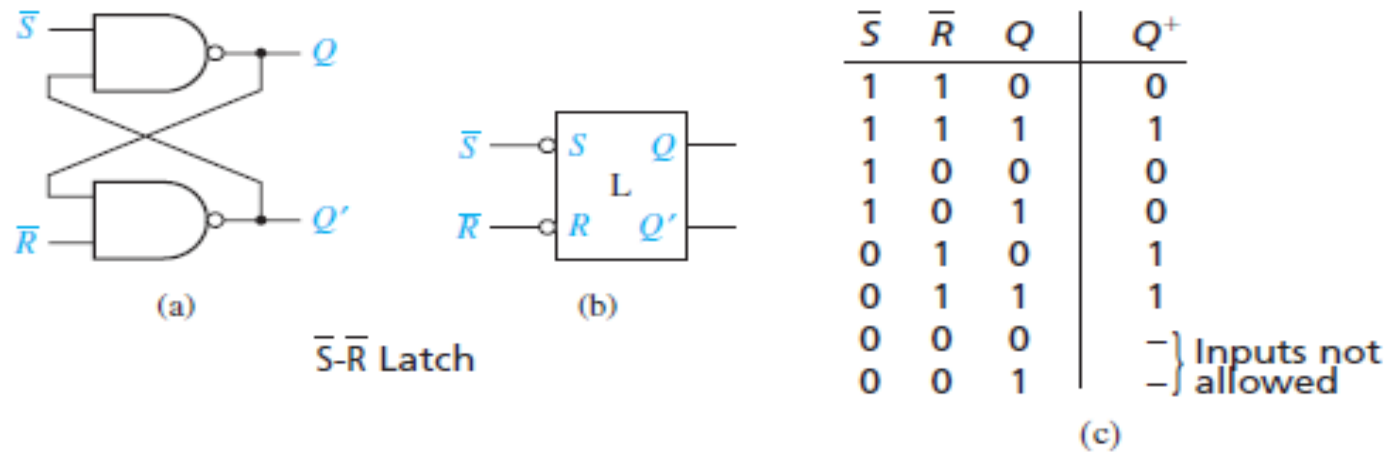- * An alternative form of the S-R latch uses NAND gates, as shown in the following Figure.



- * Applications of S-R Latch:

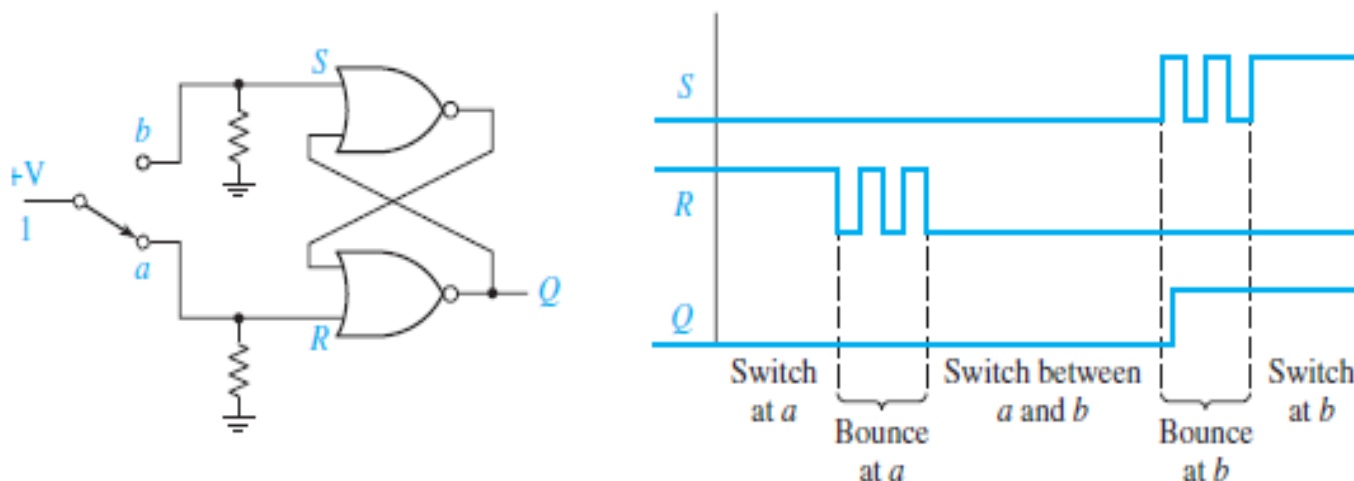




GATED D LATCH

* A gated D latch has two inputs—a data input (D) and a gate input (G).

* When $G = 0$, $S = R = 0$, so Q does not change.

* When $G = 1$ * $D = 1$, $S = 1$ and $R = 0$, so Q is set to 1 .

   * $D = 0$, $S = 0$ and $R = 1$, so Q is reset to 0 .




G	D	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

Q \ GD				
	00	01	11	10
0	0	0	1	0
1	1	1	1	0


$$Q^+ = G'Q + GD$$

EDGE TRIGGERED D FLIP-FLOP

- * A *D* flip-flop has two inputs, *D* (data) and *Clk* (clock).
- * Unlike the *D* latch, the flip-flop output changes only in response to the clock, not to a change in *D*.
- * If the output can change in response to
 - * a *0* to *1* transition on the clock input, we say that the flip-flop is triggered on the *rising edge* (or *positive edge*) of the clock.
 - * a *1* to *0* transition on the clock input, we say that the flip-flop is triggered on the *falling edge* (or *negative edge*) of the clock.
- * An *inversion bubble* on the clock input indicates a *falling-edge trigger* (Figure (b)), and no bubble indicates a rising-edge trigger (Figure (a)).
- * The term *active edge* refers to the clock edge (rising or falling) that triggers the flip-flop state change.

 

(a) Rising-edge trigger

 


(b) Falling-edge trigger

D	Q	Q^+
0	0	0
0	1	0
1	0	1
1	1	1


$$Q^+ = D$$

 (c) Truth table


Timing for
D Flip-Flop
(Falling-Edge
Trigger)



D Flip-Flop
(Rising-Edge
Trigger)

 

 
(a) Construction from two gated D latches



 (b) Timing analysis

- * A flip-flop changes state only on the active edge of the clock; the *propagation delay* (t_p) of a flip-flop is the time between the active edge of the clock and the resulting change in the output.
- * There are also timing issues associated with the D input.
 - * To function properly, the *D* input to an edge-triggered flip-flop must be held at a constant value for a period of time before and after the active edge of the clock.
 - * If D changes at the same time as the active edge, the behavior is unpredictable.


- * The amount of time that the D input must be stable before the active edge is called the *setup time* (t_{su}),
- * The amount of time that the D input must hold the same value after the active edge is the *hold time* (t_h).




- * Using these timing parameters, we can determine the minimum clock period for a circuit which will not violate the timing constraints.

- * Figure (a): Inverter has a propagation delay of 2 ns, and the flip-flop has a propagation delay of 5 ns and a setup time of 3 ns.


Determination of
Minimum Clock
Period

 


(a) Simple flip-flop circuit

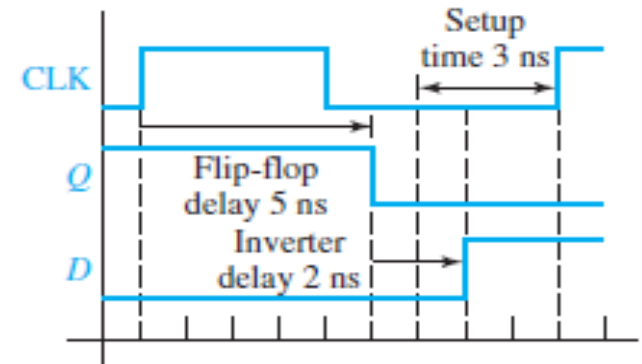

(b) Setup time not satisfied

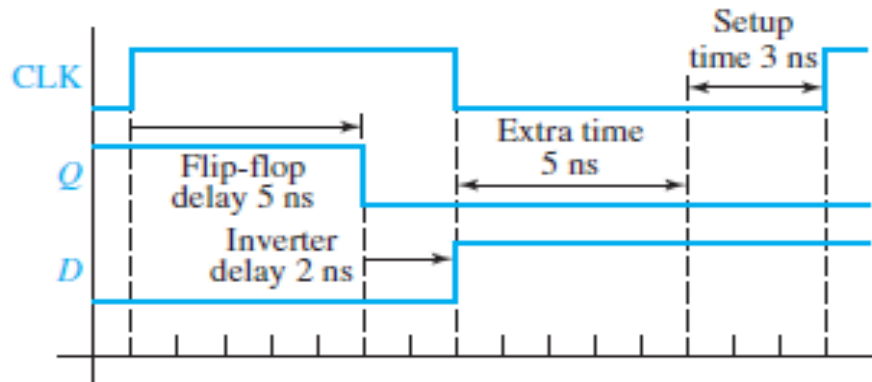


(c) Setup time satisfied

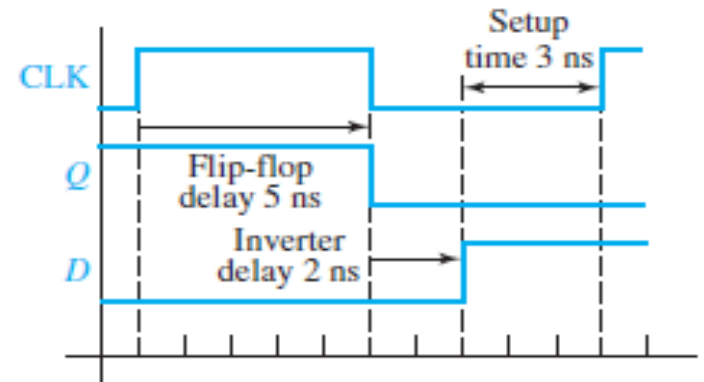

 (d) Minimum clock period

SR FLIP-FLOP


- * An S-R flip-flop is similar to an S-R latch in that $S = 1$ sets the Q output to 1, and $R = 1$ resets the Q output to 0.
- * The difference is that the flip-flop has a clock input; and the Q output can change only after an active clock edge.




Operation summary:

$S = R = 0$	No state change
$S = 1, R = 0$	Set Q to 1 (after active Ck edge)
$S = 0, R = 1$	Reset Q to 0 (after active Ck edge)
$S = R = 1$	Not allowed

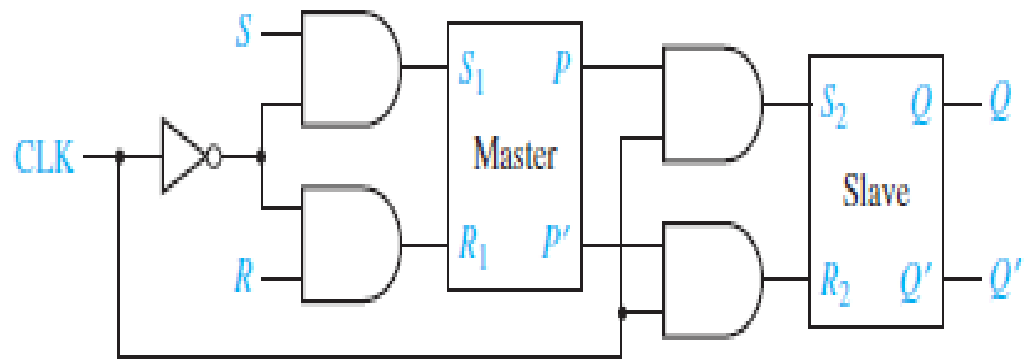* The following Figure (a) shows an S-R flip-flop constructed from two S-R latches and gates. This flip-flop changes state after the rising edge of the clock. The circuit is often referred to as a *master-slave flip-flop*.




(a) Implementation with two latches

 

(b) Timing analysis

JK FLIP-FLOP

 


(a) J-K flip-flop


$$Q^+ = JQ' + K'Q$$

J	K	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

(b) Truth table

 

(c) J-K flip-flop timing

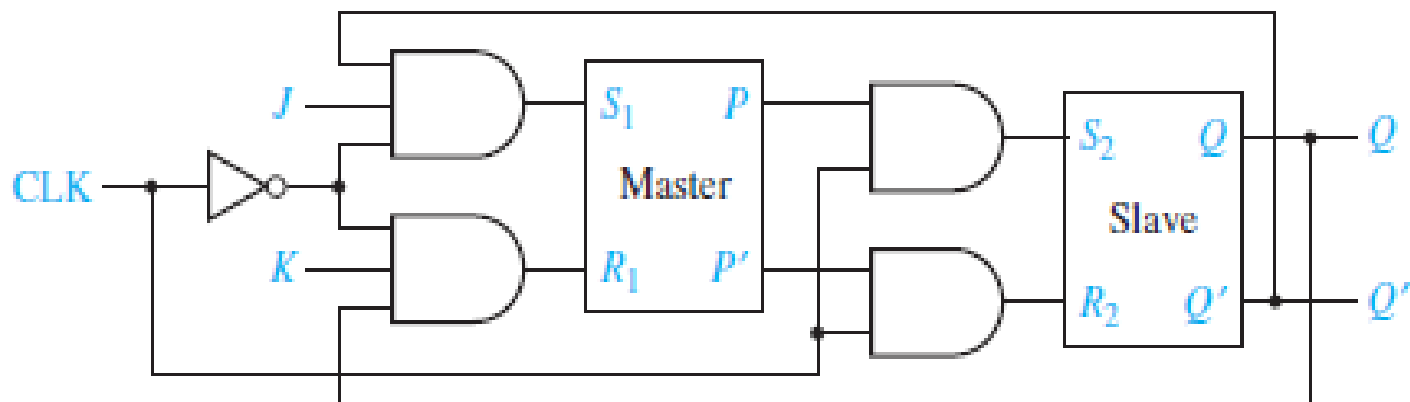

T FLIP-FLOP




(a)

T	Q	Q^+
0	0	0
0	1	1
1	0	1
1	1	0


(b)

$$Q^+ = TQ + TQ' = T \oplus Q$$

 


Timing Diagram for T Flip-Flop (Falling-Edge Trigger)

Implementation
of T Flip-Flops

 

(a) Conversion of J-K to T

 


(b) Conversion of D to T

$$Q^+ = JQ' + K'Q = TQ' + T'Q$$


$$Q^+ = Q \oplus TQ' + T'Q$$

FLIP-FLOP WITH ADDITIONAL INPUTS


D Flip-Flop with Clock Enable

 


(a) Gating the clock

 

(b) D-CE symbol

 

(c) Implementation

 


(a)

Ck	D	PreN	ClrN	Q ⁺
x	x	0	0	(not allowed)
x	x	0	1	1
x	x	1	0	0
↑	0	1	1	0
↑	1	1	1	1
0,1,↓	x	1	1	Q (no change)

(b)

 Timing Diagram for D Flip-Flop with Asynchronous Clear and Preset



- * Flip-flops often have additional inputs which can be used to set the flip-flops to an initial state independent of the clock.

* Characteristic Equations of Flip-Flops


S	R	Q^+
0	0	Q
0	1	0
1	0	1
1	1	?

D	Q	Q^+
0	0	0
0	1	0
1	0	1
1	1	1


J	K	Q^+
0	0	Q
0	1	0
1	0	1
1	1	\bar{Q}

T	Q	Q^+
0	0	0
0	1	1
1	0	1
1	1	0

SR Flip-Flop:

 

D Flip-Flop:

 

$$Q^+ = S + R'Q \text{ (SR = 0)}$$

(S-R latch or flip-flop)


$$Q^+ = GD + G'Q$$

(gated D latch)


$$Q^+ = D$$

(D flip-flop)

JK Flip-Flop:

 

T Flip-Flop:

 

$$Q^+ = T \oplus Q = TQ' + T'Q$$

$$Q^+ = D \cdot CE + Q \cdot CE'$$

(D-CE flip-flop)

$$Q^+ = JQ' + K'Q$$

(J-K flip-flop)

$$Q^+ = T \oplus Q = TQ' + T'Q$$

(T flip-flop)

* Flip-Flop as Finite State Machine


* State Transition Diagrams of SR, D, JK & T Flip-Flops

$Q \rightarrow Q_{n+1}$		S	R	J	K	D	T
0	0	0	x	0	x	0	0
0	1	1	0	1	x	1	1
1	0	0	1	x	1	0	1
1	1	x	0	x	0	1	0


Excitation Table of Flip-Flops

Homework:

 
1] Assume that the inverter in the given circuit has a propagation delay of 5 ns and the AND gate has a propagation delay of 10 ns. Draw a timing diagram for the circuit showing X, Y, and Z. Assume that X is initially 0, Y is initially 1, after 10 ns X becomes 1 for 80 ns, and then X is 0 again.



 
2] Complete the following timing diagram for the flip-flop:



 3] Complete the following timing diagram for a J-K flip-flop with a falling-edge trigger and asynchronous ClrN and PreN inputs.



 4] Complete the following timing diagram for an S-R latch. Assume Q begins at 1.



5] Convert by adding external gates: (a) a D flip-flop to a J-K flip-flop; (b) a T flip-flop to a D flip-flop; (c) a T flip-flop to a D flip-flop with clock enable.